 




UART_TX

Prepared by:

Arwa Ashraf Kantoush

TABLE OF CONTENTS

1. INTRODUCTION & OVERVIEW

- 1.1 Project Overview & Objectives
- 1.2 UART_TX Architecture Summary
- 1.3 Operational Features & Frame Transmission Sequence

2. RTL DESIGN & MODELING

- 2.1 Parity Calculator
- 2.2 Serializer
- 2.3 MUX
- 2.4 FSM
- 2.5 TOP-LEVEL MODULE

3. FUNCTIONAL VERIFICATION & TESTBENCH

4. SIMULATION & AUTOMATION

- 4.1 QuestaSim Simulation Script (run.do)
- 4.2 Simulation Waveforms

5. DESIGN CONSTRAINTS

6. ELABORATION FLOW

7. SYNTHESIS FLOW

8. IMPLEMENTATION FLOW (PLACE & ROUTE)

9. TIMING REPORT

9.1 Setup slack

9.2 Hold slack


10. LINTING

1. INTRODUCTION & OVERVIEW

1.1 Project Overview & Objectives

The Universal Asynchronous Receiver-Transmitter (UART) is a fundamental protocol for serial communication in digital and embedded systems. This project focuses on designing and verifying a parameterized **UART Transmitter (UART TX)** subsystem using synthesizable **Verilog HDL** to serialize parallel data with high reliability and timing accuracy.

1.2 UART_TX Architecture Summary

 

	Source State	Destination State	Condition
1	DATA	STOP	(!P_EN),(SER_DONE)
2	DATA	PARITY	(P_EN),(SER_DONE)
3	DATA	DATA	(!SER_DONE)
4	IDLE	IDLE	(!V_INPUT)
5	IDLE	START	(V_INPUT)
6	PARITY	STOP	
7	START	DATA	
8	STOP	IDLE	

The design comprises four core functional blocks:

- **Main Controller (FSM):** Controls transmission states (IDLE, START, DATA, PARITY, STOP) and asserts the BUSY status signal.
- **Serializer:** Converts the N -bit parallel bus into a serial bitstream and generates a completion flag (SER_DONE).
- **Parity Bit Calculator:** Generates the parity bit using reduction XOR/XNOR logic according to user configuration.
- **Multiplexer (MUX):** Directs Start, Data, Parity, or Stop/IDLE bits onto the TX_OUTPUT line.

1.3 Operational Features & Frame Transmission Sequence

- **Flexible Parity:** Supports optional parity (P_EN) with selectable Even/Odd modes (P_BIT).
- **Asynchronous Reset:** Active-low reset (RST) to instantly initialize all internal registers.
- **Single-Cycle Handshake:** Samples input data on a 1-clock-cycle pulse on V_INPUT.
- **Busy Protection:** Asserts BUSY = 1 during transmission and locks out any new data requests until the active frame finishes.
- **Idle Stability:** Maintains TX_OUTPUT = 1 during idle states to prevent false start triggers.

2. RTL DESIGN & MODELING

2.1 Parity Calculator

```
module Parity_Calculator #(
    parameter WIDTH = 8
) (
    input CLK,
    input RST,
    input [WIDTH-1:0]P_INPUT,
    input V_INPUT,
    input P_EN,
    input P_BIT,
    output reg PARITY_BIT
);

always @(posedge CLK or negedge RST) begin
    if (!RST) begin
        PARITY_BIT <= 0;
    end
    else begin
        if (V_INPUT && P_EN) begin
            if (P_BIT) begin
                PARITY_BIT <= ~^P_INPUT;
            end
            else begin
                PARITY_BIT <= ^P_INPUT;
            end
        end
    end
end

endmodule //Parity_Calculator
```

2.2 Serializer

```
module Serializer #(
    parameter WIDTH = 8
) (
    input CLK,
    input RST,
    input [WIDTH-1:0]P_INPUT,
    input V_INPUT,
    input SER_EN,
    output SER_DATA,
    output reg SER_DONE
);
reg [WIDTH-1:0]register;
reg [$clog2(WIDTH)-1:0]counter;

always @(posedge CLK or negedge RST) begin
    if (!RST) begin
        SER_DONE <= 0;
        register <= 0;
        counter <= 0;
    end
    else if (V_INPUT && !SER_EN) begin
        register <= P_INPUT;
        SER_DONE <= 0;
        counter <= 0;
    end
    else if (SER_EN) begin
        if (counter < WIDTH-2) begin
            register <= {1'b0,register[WIDTH-1:1]};
            SER_DONE <= 0;
            counter <= counter + 1;
        end
        else begin
            register <= {1'b0,register[WIDTH-1:1]};
            SER_DONE <= 1;
            counter <= 0;
        end
    end
    else begin
        SER_DONE <= 0;
    end
end

assign SER_DATA = (!RST)? 0 : register[0];

endmodule //Serializer
```

2.3 MUX

```
module MUX #(
    parameter START_BIT = 0,
    parameter STOP_BIT = 1
) (
    input SER_DATA,
    input PARITY_BIT,
    input [1:0]SEL,
    output reg TX_OUTPUT
);

always @(*) begin
    case (SEL)
        2'b00 : begin
            TX_OUTPUT = START_BIT;
        end
        2'b01 : begin
            TX_OUTPUT = SER_DATA;
        end
        2'b10 : begin
            TX_OUTPUT = PARITY_BIT;
        end
        2'b11 : begin
            TX_OUTPUT = STOP_BIT;
        end
        default : begin
            TX_OUTPUT = STOP_BIT;
        end
    endcase
end

endmodule //MUX
```

2.4 FSM

```
module FSM (  
    input CLK,  
    input RST,  
    input V_INPUT,  
    input P_EN,  
    input SER_DONE,  
    output reg SER_EN,  
    output reg BUSY,  
    output reg [1:0]SEL  
);  
localparam IDLE = 3'b000;  
localparam START = 3'b001;  
localparam DATA = 3'b010;  
localparam PARITY = 3'b011;  
localparam STOP = 3'b100;  
  
reg [2:0]cs,ns;  
  
always @(*) begin  
    case (cs)  
        IDLE : begin  
            if (V_INPUT) begin  
                ns = START;  
            end  
            else begin  
                ns = IDLE;  
            end  
        end  
        START : begin  
            ns = DATA;  
        end  
        DATA : begin  
            if (SER_DONE) begin  
                if (P_EN) begin  
                    ns = PARITY;  
                end  
                else begin  
                    ns = STOP;  
                end  
            end  
            else begin  
                ns = DATA;  
            end  
        end  
        PARITY : begin
```



```

        ns = STOP;
    end
    STOP : begin
        ns = IDLE;
    end
    default : begin
        ns = IDLE;
    end
endcase
end

always @(posedge CLK or negedge RST) begin
    if (!RST) begin
        cs <= IDLE;
    end
    else begin
        cs <= ns;
    end
end

always @(*) begin
    case (cs)
        IDLE : begin
            SER_EN = 0;
            BUSY = 0;
            SEL = 2'b11;
        end
        START : begin
            SER_EN = 0;
            BUSY = 1;
            SEL = 2'b00;
        end
        DATA : begin
            SER_EN = 1;
            BUSY = 1;
            SEL = 2'b01;
        end
        PARITY : begin
            SER_EN = 0;
            BUSY = 1;
            SEL = 2'b10;
        end
        STOP : begin
            SER_EN = 0;
            BUSY = 1;
            SEL = 2'b11;
        end
    end
end

```

```
        default : begin
            SER_EN = 0;
            BUSY = 0;
            SEL = 2'b11;
        end
    endcase
end

endmodule //FSM
```

2.5 TOP-LEVEL MODULE

```
module UART_TX #(
    parameter WIDTH = 8
) (
    input CLK,
    input RST,
    input [WIDTH-1:0]P_INPUT,
    input V_INPUT,
    input P_EN,
    input P_BIT,
    output TX_OUTPUT,
    output BUSY
);
wire PARITY_BIT;
wire SER_EN;
wire SER_DATA;
wire SER_DONE;
wire [1:0]SEL;

Parity_Calculator #(.WIDTH(WIDTH)) dut1 (
    .CLK(CLK),
    .RST(RST),
    .P_INPUT(P_INPUT),
    .V_INPUT(V_INPUT),
    .P_EN(P_EN),
    .P_BIT(P_BIT),
    .PARITY_BIT(PARITY_BIT)
);

Serializer #(.WIDTH(WIDTH)) dut2 (
    .CLK(CLK),
    .RST(RST),
    .P_INPUT(P_INPUT),
    .V_INPUT(V_INPUT),
    .SER_EN(SER_EN),
    .SER_DATA(SER_DATA),
    .SER_DONE(SER_DONE)
);

MUX dut3 (
    .SER_DATA(SER_DATA),
    .PARITY_BIT(PARITY_BIT),
    .SEL(SEL),
    .TX_OUTPUT(TX_OUTPUT)
);
```

```
FSM dut (  
    .CLK(CLK),  
    .RST(RST),  
    .V_INPUT(V_INPUT),  
    .P_EN(P_EN),  
    .SER_DONE(SER_DONE),  
    .SER_EN(SER_EN),  
    .BUSY(BUSY),  
    .SEL(SEL)  
);  
  
endmodule //TOP
```

3. FUNCTIONAL VERIFICATION & TESTBENCH

```
module UART_TX_tb ();
parameter WIDTH = 8;
reg CLK;
reg RST;
reg [WIDTH-1:0]P_INPUT;
reg V_INPUT;
reg P_EN;
reg P_BIT;
wire TX_OUTPUT;
reg TX_OUTPUT_exp;
wire BUSY;
reg BUSY_exp;

UART_TX #(.WIDTH(WIDTH)
) dut ( .CLK(CLK),
        .RST(RST),
        .P_INPUT(P_INPUT),
        .V_INPUT(V_INPUT),
        .P_EN(P_EN),
        .P_BIT(P_BIT),
        .TX_OUTPUT(TX_OUTPUT),
        .BUSY(BUSY)
);

initial begin
    CLK = 1;
    forever begin
        #1 CLK = ~CLK;
    end
end

integer i;
initial begin
    RST = 0;
    P_INPUT = 8'b0000_0000; V_INPUT = 0; P_EN = 0; P_BIT = 0;
    TX_OUTPUT_exp = 1; BUSY_exp = 0;
    @(negedge CLK);
    if (TX_OUTPUT !== TX_OUTPUT_exp || BUSY !== BUSY_exp)
begin
    $display("ERROR!");
    //$stop;
end
end
```

```

RST = 1;
P_INPUT = 8'b1010_0101; V_INPUT = 1; P_EN = 0; P_BIT = 0;
for (i = 0 ; i < 10 ; i = i + 1) begin
    if (i==0) begin
        TX_OUTPUT_exp = 0; BUSY_exp = 1;
    end
    else if (i<9) begin
        TX_OUTPUT_exp = P_INPUT[i-1]; BUSY_exp = 1;
    end
    else begin
        TX_OUTPUT_exp = 1; BUSY_exp = 1;
    end
    @(negedge CLK);
    V_INPUT = 0;
    if (TX_OUTPUT != TX_OUTPUT_exp || BUSY != BUSY_exp)
begin
        $display("ERROR!");
        //$stop;
    end
end

TX_OUTPUT_exp = 1; BUSY_exp = 0;
@(negedge CLK);
if (TX_OUTPUT != TX_OUTPUT_exp || BUSY != BUSY_exp)
begin
    $display("ERROR!");
    //$stop;
end

P_INPUT = 8'b1010_0101; V_INPUT = 1; P_EN = 1; P_BIT = 0;
for (i = 0 ; i < 11 ; i = i + 1) begin
    if (i==0) begin
        TX_OUTPUT_exp = 0; BUSY_exp = 1;
    end
    else if (i<9) begin
        TX_OUTPUT_exp = P_INPUT[i-1]; BUSY_exp = 1;
    end
    else if (i<10) begin
        TX_OUTPUT_exp = ^P_INPUT; BUSY_exp = 1;
    end
    else begin
        TX_OUTPUT_exp = 1; BUSY_exp = 1;
    end
    @(negedge CLK);
    V_INPUT = 0;
    if (TX_OUTPUT != TX_OUTPUT_exp || BUSY != BUSY_exp)
begin

```

```

        $display("ERROR!");
        //$stop;
    end
end

TX_OUTPUT_exp = 1; BUSY_exp = 0;
@(negedge CLK);
if (TX_OUTPUT != TX_OUTPUT_exp || BUSY != BUSY_exp)
begin
    $display("ERROR!");
    //$stop;
end

P_INPUT = 8'b1010_0101; V_INPUT = 1; P_EN = 1; P_BIT = 1;
for (i = 0 ; i < 11 ; i = i + 1) begin
    if (i==0) begin
        TX_OUTPUT_exp = 0; BUSY_exp = 1;
    end
    else if (i<9) begin
        TX_OUTPUT_exp = P_INPUT[i-1]; BUSY_exp = 1;
    end
    else if (i<10) begin
        TX_OUTPUT_exp = ~^P_INPUT; BUSY_exp = 1;
    end
    else begin
        TX_OUTPUT_exp = 1; BUSY_exp = 1;
    end
    @(negedge CLK);
    V_INPUT = 0;
    if (TX_OUTPUT != TX_OUTPUT_exp || BUSY != BUSY_exp)
begin
    $display("ERROR!");
    //$stop;
end
end

TX_OUTPUT_exp = 1; BUSY_exp = 0;
@(negedge CLK);
if (TX_OUTPUT != TX_OUTPUT_exp || BUSY != BUSY_exp)
begin
    $display("ERROR!");
    //$stop;
end
$stop;
end

initial begin

```


```
    $monitor("CLK=%b,RST=%b,P_INPUT=%b,V_INPUT=%b,P_EN=%b,P_BIT=%b,TX_OUTPUT=%b,TX_OUTPUT_exp=%b,BUSY=%b,BUSY_exp=%b",  
            CLK,RST,P_INPUT,V_INPUT,P_EN,P_BIT,TX_OUTPUT,TX_OUTPUT_exp,BUSY,BUSY_exp);  
end  
  
endmodule //UART_TX_tb
```


4. SIMULATION & AUTOMATION

4.1 QuestaSim Simulation Script (run.do)

```
vlib work
vlog Parity_Calculator.v Serializer.v FSM.v MUX.v UART_TX.v
UART_TX_tb.v
vsim -voptargs=+acc work.UART_TX_tb
add wave *
run -all
#quit -sim
```

4.2 Simulation Waveforms

 

5. DESIGN CONSTRAINTS


```
# ---- Clock definition ----
create_clock -name CLK -period 20.000 [get_ports CLK]

# ---- Reset ----
set_false_path -from [get_ports RST]


# ---- Input delays ----
set_input_delay -clock CLK -max 3.000 [get_ports {P_INPUT[*]}]
set_input_delay -clock CLK -min 0.500 [get_ports {P_INPUT[*]}]
set_input_delay -clock CLK -max 3.000 [get_ports V_INPUT]
set_input_delay -clock CLK -min 0.500 [get_ports V_INPUT]
set_input_delay -clock CLK -max 3.000 [get_ports {P_EN P_BIT}]
set_input_delay -clock CLK -min 0.500 [get_ports {P_EN P_BIT}]

# ---- Output delays ----
set_output_delay -clock CLK -max 2.000 [get_ports TX_OUTPUT]
set_output_delay -clock CLK -min 0.500 [get_ports TX_OUTPUT]
set_output_delay -clock CLK -max 2.000 [get_ports BUSY]
set_output_delay -clock CLK -min 0.500 [get_ports BUSY]
```


6. ELABORATION FLOW

 

7. SYNTHESIS FLOW

 


8. IMPLEMENTATION FLOW (PLACE & ROUTE)

 

9. TIMING REPORT

Setup Times						
	Data Port	Clock Port	Rise	Fall	Clock Edge	Clock Reference
1	P_BIT	CLK	2.946	3.322	Rise	CLK
2	P_EN	CLK	2.069	2.418	Rise	CLK
3	✓ P_INPUT[*]	CLK	4.149	4.480	Rise	CLK
1	P_INPUT[0]	CLK	3.547	3.904	Rise	CLK
2	P_INPUT[1]	CLK	3.573	3.938	Rise	CLK
3	P_INPUT[2]	CLK	3.530	3.882	Rise	CLK
4	P_INPUT[3]	CLK	3.446	3.812	Rise	CLK
5	P_INPUT[4]	CLK	3.655	4.022	Rise	CLK
6	P_INPUT[5]	CLK	4.149	4.480	Rise	CLK
7	P_INPUT[6]	CLK	3.750	4.133	Rise	CLK
8	P_INPUT[7]	CLK	3.759	4.124	Rise	CLK
9	V_INPUT	CLK	3.917	4.226	Rise	CLK

9.1 Setup slack

 


Slow 1200mV 125C Model								
Command Info		Summary of Paths						
	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Clock Skew	Data Delay
1	10.390	Parity_Calculator:dut1 PARITY_BIT	TX_OUTPUT	CLK	CLK	20.000	-2.397	5.213
2	10.395	FSM:dut cs.PARITY	TX_OUTPUT	CLK	CLK	20.000	-2.397	5.208
3	10.513	Serializer:dut2 register[0]	TX_OUTPUT	CLK	CLK	20.000	-2.399	5.088
4	10.657	FSM:dut cs.DATA	TX_OUTPUT	CLK	CLK	20.000	-2.397	4.946
5	10.868	FSM:dut cs.START	TX_OUTPUT	CLK	CLK	20.000	-2.397	4.735
6	11.148	FSM:dut cs.DATA	TX_OUTPUT	CLK	CLK	20.000	-2.397	4.455
7	11.626	FSM:dut cs.IDLE	BUSY	CLK	CLK	20.000	-2.397	3.977
8	12.520	P_INPUT[5]	Parity...TY_BIT	CLK	CLK	20.000	2.307	6.804
9	12.774	V_INPUT	Seriali...nter[1]	CLK	CLK	20.000	2.307	6.550
10	12.774	V_INPUT	Seriali...nter[0]	CLK	CLK	20.000	2.307	6.550

Path #1: Setup slack is 10.390

Path Summary		Statistics	Data Path	Waveform	Extra Fitter Information
Property	Value				
1 From Node	Parity_Calculator:dut1 PARITY_BIT				
2 To Node	TX_OUTPUT				
3 Launch Clock	CLK				
4 Latch Clock	CLK				
5 Data Arrival Time	7.610				
6 Data Required Time	18.000				
7 Slack	10.390				

9.2Hold slack

 

Slow 1200mV 125C Model								
Command Info		Summary of Paths						
	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Clock Skew	Data Delay
1	0.428	Parity_Calculator:dut1 PARITY_BIT	Parity...TY_BIT	CLK	CLK	0.000	0.075	0.692
2	0.428	Serializer:dut2 register[7]	Seriali...ster[7]	CLK	CLK	0.000	0.075	0.692
3	0.428	FSM:dut cs.DATA	FSM:d...DATA	CLK	CLK	0.000	0.075	0.692
4	0.428	Serializer:dut2 counter[1]	Seriali...nter[1]	CLK	CLK	0.000	0.075	0.692
5	0.428	Serializer:dut2 counter[2]	Seriali...nter[2]	CLK	CLK	0.000	0.075	0.692
6	0.428	FSM:dut cs.IDLE	FSM:d...IDLE	CLK	CLK	0.000	0.075	0.692
7	0.429	Serializer:dut2 counter[0]	Seriali...nter[0]	CLK	CLK	0.000	0.075	0.693
8	0.442	FSM:dut cs.STOP	FSM:d...IDLE	CLK	CLK	0.000	0.075	0.706
9	0.443	Serializer:dut2 register[6]	Seriali...ster[5]	CLK	CLK	0.000	0.075	0.707
10	0.445	Serializer:dut2 register[1]	Seriali...ster[0]	CLK	CLK	0.000	0.075	0.709

Path #10: Hold slack is 0.445

Path Summary	Statistics	Data Path	Waveform	Extra Fitter Information
	Property	Value		
1	From Node	Serializer:dut2 register[1]		
2	To Node	Serializer:dut2 register[0]		
3	Launch Clock	CLK		
4	Latch Clock	CLK		
5	Data Arrival Time	3.018		
6	Data Required Time	2.573		
7	Slack	0.445		

10. LINTING

The screenshot displays the Questa lint tool interface. The top pane shows the Verilog source code for the `UART_TX` module. The code defines inputs `CLK`, `RST`, `P_INPUT` (width 8), `V_INPUT`, `P_EN`, and outputs `TX_OUTPUT`, `BUSY`. It includes a `Parity_calculator` block and a `Serializer` block. The bottom pane shows the lint checks results, with a single warning: `parameter_name_duplicate` for `Parity_Calcul...`. The message states: "Same parameter name is used in more than one mod...". The bottom status bar shows the lint summary: "Total: 1 Selected: 0".